

Olin College of Engineering

ENGR2410 – Signals and Systems

Reference 2

Definitions

Linear system:

$$\begin{aligned} \text{If } x_1 \rightarrow \boxed{L} \rightarrow y_1 \quad \text{and} \quad x_2 \rightarrow \boxed{L} \rightarrow y_2, \\ \text{then } ax_1 + bx_2 \rightarrow \boxed{L} \rightarrow ay_1 + by_2. \end{aligned}$$


Time-invariant system:

$$\begin{aligned} \text{If } x_1(t) \rightarrow \boxed{TI} \rightarrow y_1(t) \\ \text{then } x_1(t - T) \rightarrow \boxed{TI} \rightarrow y_1(t - T). \end{aligned}$$

Eigenfunctions

$$e^{st} \rightarrow \boxed{LTI} \rightarrow \underbrace{H(s)}_{\text{transfer function}} \underbrace{e^{st}}_{\text{eigenfunction}}$$

Example:

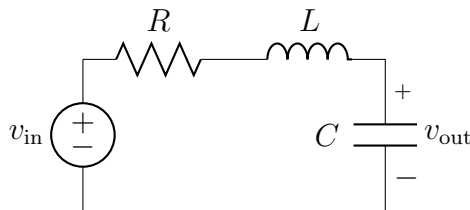

If $v_{in} = e^{st}$ in the series RLC circuit above, when know that $v_{out} = H(s)e^{st}$. Find $H(s)$ by substituting in the differential equation:

$$\begin{aligned} \ddot{v}_o + 2\alpha\dot{v}_o + \omega_0^2 v_o &= \omega_0^2 v_i \\ H(s)s^2 e^{st} + 2\alpha H(s)s e^{st} + \omega_0^2 H(s)e^{st} &= \omega_0^2 e^{st} \\ H(s)(s^2 + 2\alpha s + \omega_0^2) &= \omega_0^2 \\ H(s) &= \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2} \end{aligned}$$

Sinusoidal Steady State

A special (but important) case is when $s = j\omega$ such that the input is $e^{j\omega t}$, a complex exponential. By Euler's Equation,

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t).$$

We can “construct” the cosine function using a linear combination of two complex exponentials:

$$\cos(\omega t) = \frac{1}{2}(e^{j\omega t} + e^{-j\omega t}).$$

By linearity,

$$\cos \omega t \rightarrow \boxed{LTI} \rightarrow \text{output}$$

is equivalent to

$$\begin{aligned} \frac{1}{2}e^{j\omega t} &\rightarrow \boxed{LTI} \rightarrow \frac{1}{2}H(j\omega)e^{j\omega t} \\ &+ \\ \frac{1}{2}e^{-j\omega t} &\rightarrow \boxed{LTI} \rightarrow \frac{1}{2}H(-j\omega)e^{-j\omega t} \end{aligned}$$

Therefore, the output is

$$\frac{1}{2}H(j\omega)e^{j\omega t} + \frac{1}{2}H(-j\omega)e^{-j\omega t}.$$

If H is *holomorphic*, then $H(-j\omega) = H^*(j\omega)$, where the asterisk denotes the complex conjugate. Likely all the functions you will use will be holomorphic.

In polar form,

$$\begin{aligned} H(j\omega) &= |H(j\omega)|e^{j\angle H(j\omega)} \\ H(-j\omega) &= H^*(j\omega) = |H(j\omega)|e^{-j\angle H(j\omega)} \end{aligned}$$

So the output of the system is

$$\begin{aligned} &\frac{1}{2}|H(j\omega)|e^{j\angle H(j\omega)}e^{j\omega t} + \frac{1}{2}|H(j\omega)|e^{-j\angle H(j\omega)}e^{-j\omega t} \\ &= |H(j\omega)| \frac{e^{j(\omega t + \angle H(j\omega))} + e^{-j(\omega t + \angle H(j\omega))}}{2} \\ &= |H(j\omega)| \cos(\omega t + \angle H(j\omega)). \end{aligned}$$

The general solution for the sinusoidal steady state is

$$\boxed{\cos \omega t \rightarrow \boxed{LTI} \rightarrow |H(j\omega)| \cos(\omega t + \angle H(j\omega))}$$

Note:

- (i) the output has the same frequency as the input
- (ii) the output is scaled and shifted by $H(j\omega)$

For example, the transfer function of the series RLC circuit is

$$H(j\omega) = \frac{\omega_0^2}{-\omega^2 + j2\alpha\omega + \omega_0^2}$$

Its magnitude and phase are

$$|H(j\omega)| = \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\alpha\omega)^2}}, \quad \angle H(j\omega) = -\tan^{-1} \left(\frac{2\alpha\omega}{\omega_0^2 - \omega^2} \right).$$

Therefore, if

$$v_i = V \cos(\omega t),$$

then

$$v_o = V \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + (2\alpha\omega)^2}} \cos \left[\omega t - \tan^{-1} \left(\frac{2\alpha\omega}{\omega_0^2 - \omega^2} \right) \right].$$

Bode Plot

The plot of $|H(j\omega)|$ and $\angle H(j\omega)$ as a function of ω completely describes $H(j\omega)$. A Bode plot shows $\log |H(j\omega)|$ as a function of $\log \omega$ for the magnitude and $\angle H(j\omega)$ as a function of $\log \omega$ for the angle.

In order to sketch a Bode plot, we consider the asymptotes at both extremes. For example, the transfer function of the series RLC circuit is

$$H(j\omega) = \frac{\omega_0^2}{-\omega^2 + j2\alpha\omega + \omega_0^2}$$

$$\text{If } \omega \rightarrow 0, \text{ then } H(j\omega) \approx \frac{\omega_0^2}{\omega_0^2} = 1 \quad \text{and} \quad |H(j\omega)| = 1, \quad \angle H(j\omega) = 0$$

$$\text{If } \omega \rightarrow \infty, \text{ then } H(j\omega) \approx -\frac{\omega_0^2}{\omega^2} \quad \text{and} \quad |H(j\omega)| = \frac{\omega_0^2}{\omega^2}, \quad \angle H(j\omega) = \pm\pi$$

In the magnitude plot, the two lines intersect when $1 = \frac{\omega_0^2}{\omega^2}$, or $\omega = \omega_0$, the resonant frequency. If we substitute the resonant frequency into the transfer function, we find

$$H(j\omega_0) = \frac{\omega_0^2}{j2\alpha\omega_0} = -j\frac{\omega_0}{2\alpha} \quad \text{and} \quad |H(j\omega)| = \frac{\omega_0}{2\alpha} \triangleq Q, \quad \angle H(j\omega) = -\frac{\pi}{2}.$$

The variable Q is called the quality factor and is widely used to characterize 2nd order systems. The Bode plot is shown below.

