

# Olin College of Engineering

## ENGR2410 – Signals and Systems

### Reference 3

#### Standard forms

When working with symbolic expressions, pattern recognition plays a major role. Force yourself to always follow standard forms, where highest order derivate or term in a polynomial does not have a coefficient, for example,

$$\ddot{v}_{out} + 2\alpha\dot{v}_{out} + \omega_0^2 v_{out} = \omega_0^2 v_{in}$$


$$H(s) = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$$

$$H(s) = \frac{1/\tau}{s + 1/\tau}$$

Identify known terms (especially time constants and frequencies), group and keep them together, and write them in the typical order:  $RC$ ,  $LC$ ,  $L/R$ .
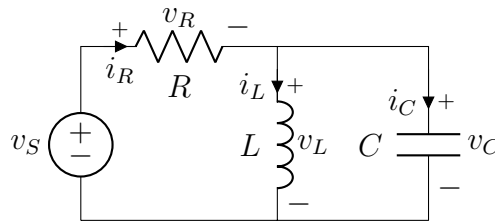
#### Circuits as LTI systems

So far we have only used circuit diagrams to derive a differential equation. We can use them directly to our advantage by using linearity.



Circuit diagrams are graphical ways to represent differential equations. For example, the circuit above satisfies the conditions:

KVL

$$v_S(t) = v_R(t) + v_L(t)$$

$$v_L(t) = v_C(t)$$

KCL

$$i_R(t) = i_L(t) + i_C(t)$$

Device laws

$$v_R(t) = Ri_R(t)$$

$$v_L(t) = L \frac{di_L}{dt}$$

$$i_C(t) = C \frac{dv_C}{dt}$$

Linearity implies that if any one of

$$v_R(t) = V_R e^{st} \quad v_L(t) = V_L e^{st} \quad v_C(t) = V_C e^{st}$$

is true, then all the others must be true also. As a result, exponential amplitudes satisfy KVL and KCL:

$$v_S(t) = v_R(t) + v_L(t)$$

$$V_S e^{st} = V_R e^{st} + V_L e^{st}$$

$$V_S = V_R + V_L$$

Exponential amplitudes satisfy device laws as *algebraic* equations:

$$v_C(t) = V_C e^{st}$$


$$i_C(t) = I_C e^{st}$$

$$i_C = C \dot{v}_C(t)$$

$$I_C e^{st} = C V_C s e^{st}$$


$$Z_C = \frac{V_C}{I_C} = \frac{1}{Cs}$$

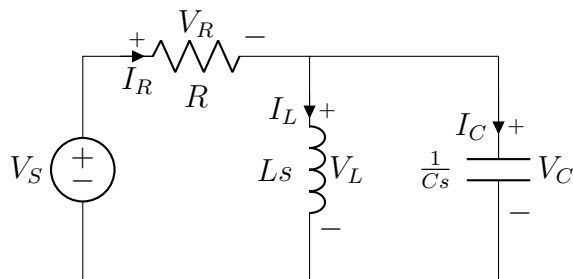$Z_C$  is called *impedance*. The impedance of a resistor  $R$  is  $Z_R = R$ . The impedance of an inductor is  $Z_L = Ls$ . Therefore, linear circuits can be written in terms of impedances and exponential amplitudes.


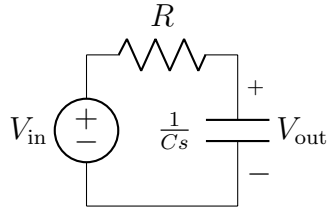
## Manipulating impedances


Impedances can be treated as resistors, including all the usual resistor techniques: series, parallel, voltage dividers, current dividers and so forth.



$$V_{out} = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} V_{in}$$

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

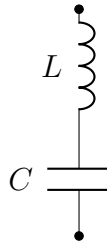Impedances can also be computed for combinations of elements.



$$Z_{eq} = Ls + \frac{1}{Cs} = \frac{LCs^2 + 1}{Cs} = \frac{s^2 + \frac{1}{LC}}{\frac{s}{L}}$$

In particular, the impedance at the resonant frequency  $\omega_0 = 1/\sqrt{LC}$  of each element is

$$Z_L = jL\omega = jL \frac{1}{\sqrt{LC}} = j\sqrt{\frac{L}{C}}$$

$$Z_C = -j \frac{1}{C\omega} = -j \frac{\sqrt{LC}}{C} = -j\sqrt{\frac{L}{C}}$$

and  $Z_L + Z_C = 0$  at resonance.