

Olin College of Engineering
ENGR2410 – Signals and Systems

Quiz 3 Solutions

Instructions


- A. Collaboration is not allowed on quizzes.
- B. Students may only use a page of notes and the tables from the website during the quizzes.
- C. Time is limited to one continuous hour.
- D. Quizzes are due at the beginning of lecture on Thursday.
- E. Late or missed quizzes will be given a score of zero. Any excuses must come directly from the Office of Student Life.
- F. The two lowest quiz scores will be eliminated to allow for unforeseeable circumstances.
- G. In case of doubt, students are expected to base their behavior on the values expressed in the Honor Code.

Name:

Start time:

Problem 1 (10 points)

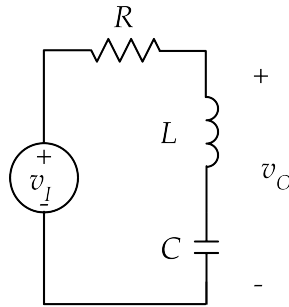A. Find the transfer function for the circuit shown below using impedances.



Solution:

$$H(s) = \frac{V_O}{V_I} = \frac{Ls + \frac{1}{Cs}}{R + Ls + \frac{1}{Cs}}$$

$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{L/R}s + \frac{1}{LC}}$$

$$\omega_0^2 = \frac{1}{LC} \quad \alpha = \frac{1}{2L/R}$$

$$H(j\omega) = \frac{\omega_0^2 - \omega^2}{\omega_0^2 - \omega^2 + j2\alpha\omega}$$

B. Sketch *only* the Bode plot of the magnitude of $H(s)$.


Solution:

$$\omega \rightarrow 0 \quad H(j\omega) \approx 1$$

$$\omega \rightarrow \infty \quad H(j\omega) \approx 1$$

At resonance, $\omega = \omega_0$, and the series LC acts like a short.
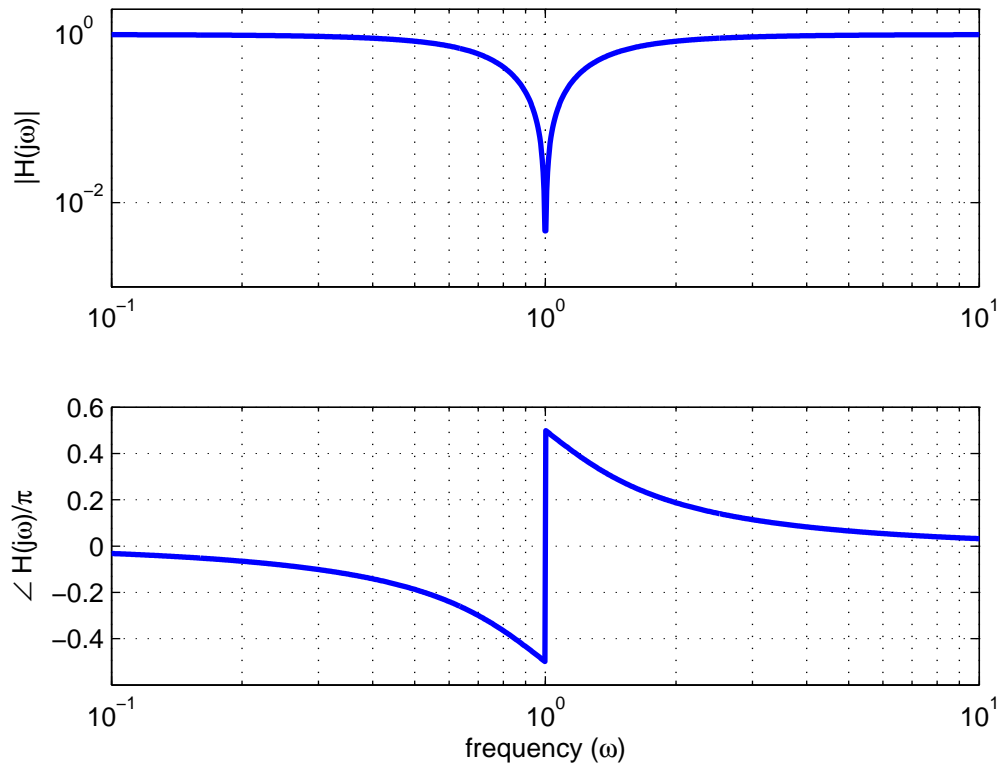
$$\omega = \omega_0 \quad H(j\omega) = 0$$




Only the magnitude is required for the quiz.

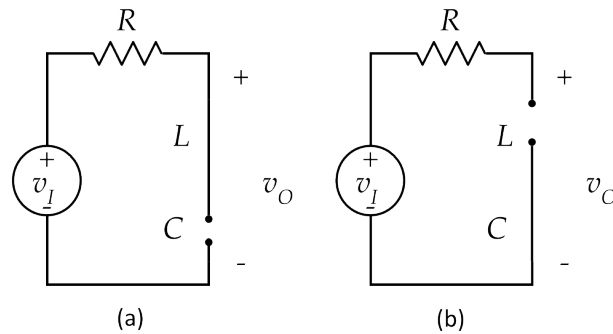- C. Recall that at low frequencies a capacitor may be replaced with an open circuit and an inductor may be replaced with a short circuit and the inverse is true at high frequencies. Draw equivalent circuits for low frequencies and high frequencies. Use them to verify the extremes of the Bode plot.


Solution:

The left circuit depicts how the original circuit behaves at low frequencies when the capacitor acts like an open circuit and the inductor acts like a short. The right circuit depicts the original circuit at high frequencies when the capacitor acts like a short and the inductor acts like an open circuit. The result in either of these cases is that $v_O = v_I$ as expected, since current flows through R.



D. Draw an equivalent circuit at resonance.

Solution:

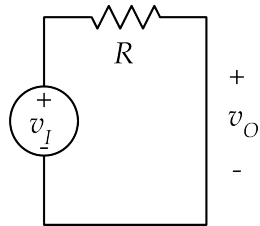

At resonance, $v_O = 0$, or $H(s) = 0$.

Course feedback

Feel free to send any additional feedback directly to us.

Name (optional):

- A. End time: How long did the quiz take you?
- B. Was the quiz a fair measure of your understanding?
- C. Was the assignment effective preparation for the quiz?
- D. Is the Monday session effective?
- E. Are the connections between lecture, assignment and quiz clear?
- F. Are the objectives of the course clear? Do you feel you are making progress towards those objectives?
- G. Anything else?

Assignment grades

Date:

Assignment number:

Group member 1:

Grade:

Group member 2:

Grade:

Group member 3:

Grade: