

Olin College of Engineering
ENGR2410 – Signals and Systems

Quiz 2

Instructions


- A. Collaboration is not allowed on quizzes.
- B. Students may only use a page of notes and the tables from the website during the quizzes.
- C. Time is limited to one continuous hour.
- D. Quizzes are due at the beginning of lecture on Thursday.
- E. Late or missed quizzes will be given a score of zero. Any excuses must come directly from the Office of Student Life.
- F. The two lowest quiz scores will be eliminated to allow for unforeseeable circumstances.
- G. In case of doubt, students are expected to base their behavior on the values expressed in the Honor Code.

Name:

Start time:

Problem 1 (10 points)

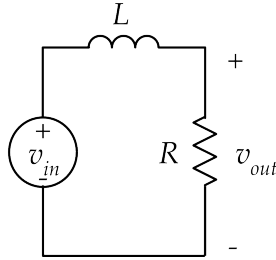- A. Find v_{out} in the circuit below if $v_{in} = V \cos \omega t$. You may assume all transients have disappeared.



Solution:

$$\dot{v}_{out} + \frac{1}{L/R} v_{out} = \frac{1}{L/R} v_{in}$$

$$v_{in} = e^{j\omega t} \quad v_{out} = H(j\omega) e^{j\omega t}$$

$$H(j\omega) j\omega e^{j\omega t} + \frac{1}{L/R} H(j\omega) e^{j\omega t} = \frac{1}{L/R} e^{j\omega t}$$

$$H(j\omega) = \frac{\frac{1}{L/R}}{j\omega + \frac{1}{L/R}} \quad |H(j\omega)| = \frac{\frac{1}{L/R}}{\sqrt{\omega^2 + \frac{1}{(L/R)^2}}} \quad \angle H(j\omega) = -\tan^{-1} \omega L/R$$

$$v_{out} = V \frac{\frac{1}{L/R}}{\sqrt{\omega^2 + \frac{1}{(L/R)^2}}} \cos(\omega t - \tan^{-1} \omega L/R)$$

B. Sketch the Bode plot of the circuit using asymptotic approximations.


Solution:

$$H(j\omega) = \frac{\frac{1}{L/R}}{j\omega + \frac{1}{L/R}}$$

$$\text{If } \omega \rightarrow 0, \text{ then } H(j\omega) \approx \frac{\frac{1}{L/R}}{\frac{1}{L/R}} = 1 \quad \text{and} \quad |H(j\omega)| = 1, \quad \angle H(j\omega) = 0$$

$$\text{If } \omega \rightarrow \infty, \text{ then } H(j\omega) \approx \frac{\frac{1}{L/R}}{j\omega} \quad \text{and} \quad |H(j\omega)| = \frac{1}{\omega L/R}, \quad \angle H(j\omega) = -\frac{\pi}{2}$$

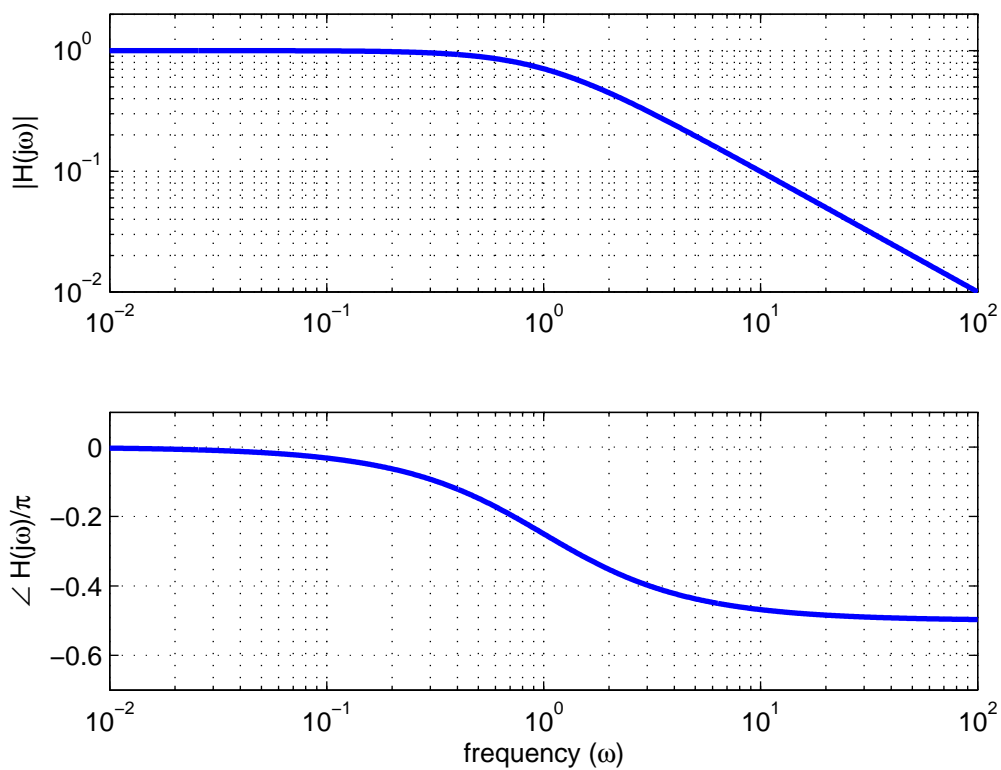Intersection at $\omega = \frac{1}{L/R}$. Since this system is first order, the Bode plot transitions smoothly at the intersection.



Course feedback

Feel free to send any additional feedback directly to us.

Name (optional):

- A. End time: How long did the quiz take you?
- B. Was the quiz a fair measure of your understanding?
- C. Was the assignment effective preparation for the quiz?
- D. Is the Monday session effective?
- E. Are the connections between lecture, assignment and quiz clear?
- F. Are the objectives of the course clear? Do you feel you are making progress towards those objectives?
- G. Anything else?

Assignment grades

Date:

Assignment number:

Group member 1:

Grade:

Group member 2:

Grade:

Group member 3:

Grade: