

Olin College of Engineering
ENGR2410 – Signals and Systems

Assignment 3

Problem 1

- A. Find the equivalent impedance of a series RLC combination.

Solution:

$$\begin{aligned}Z &= R + Ls + \frac{1}{Cs} \\Z &= \frac{s^2 + \frac{1}{L/R}s + \frac{1}{LC}}{s/L} \\Z &= \frac{1}{Cs} \left(\frac{s^2 + \frac{1}{L/R}s + \frac{1}{LC}}{\frac{1}{LC}} \right) \\Z &= \frac{L \left(s^2 + \frac{1}{L/R}s + \frac{1}{LC} \right)}{s}\end{aligned}$$

- B. Find an expression for the quality factor Q of the series RLC in terms of the characteristic impedance $Z_0 = \sqrt{L/C}$. Recall that Q is defined as $\frac{\omega_0}{2\alpha}$.

Solution:

$$Q = \frac{1}{\sqrt{LC}} L/R = \frac{\sqrt{L/C}}{R}$$

- C. Find a condition for R such that $Q \gg 1$. In the limit, is R acting more like a short or an open circuit?

Solution:

$$R \ll \sqrt{L/C}$$

R is approaching a short.

D. Repeat the previous three parts for the parallel RLC combination.

Solution:

$$Z = R || Ls || \frac{1}{Cs} = R || \frac{Ls}{LCs^2 + 1} = \frac{s/C}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$$Z = \frac{1}{C} \cdot \frac{s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$


$$Q = \frac{1}{\sqrt{LC}}RC = \frac{R}{\sqrt{L/C}}$$

$$R \gg \sqrt{L/C}$$

R is approaching an open.

Problem 2

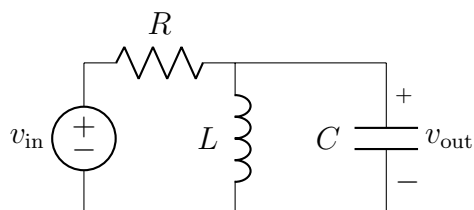A. Find the transfer function for the parallel RLC circuit using impedances.



Solution:

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{Ls || \frac{1}{Cs}}{R + Ls || \frac{1}{Cs}}$$

$$H(s) = \frac{\frac{Ls}{LCs^2+1}}{R + \frac{Ls}{LCs^2+1}}$$

$$H(s) = \frac{Ls}{RLCs^2 + Ls + R}$$

$$H(s) = \frac{\frac{1}{RC}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

- B. Show that at low frequencies a capacitor may be replaced with an open circuit and an inductor may be replaced with a short circuit. Show that the inverse is true at high frequencies.

Solution:

The complex impedance of a capacitor is $\frac{1}{Cj\omega}$. The impedance of the capacitor is related inversely to frequency. At low frequencies $\omega \rightarrow 0$, the impedance of the capacitor is really large and the capacitor acts like an open circuit. At high frequencies $\omega \rightarrow \infty$, the impedance of the capacitor is really small and the capacitor acts like a short circuit.

$$\lim_{\omega \rightarrow 0} \frac{1}{Cj\omega} = \infty$$

$$\lim_{\omega \rightarrow \infty} \frac{1}{Cj\omega} = 0$$

The complex impedance of an inductor is $Lj\omega$. The impedance of the inductor is related directly to frequency. At low frequencies $\omega \rightarrow 0$, the impedance of the inductor is really small and the inductor acts like a short circuit. At high frequencies $\omega \rightarrow \infty$, the impedance of the inductor is really large and the inductor acts like an open circuit.


$$\lim_{\omega \rightarrow 0} Lj\omega = 0$$

$$\lim_{\omega \rightarrow \infty} Lj\omega = \infty$$

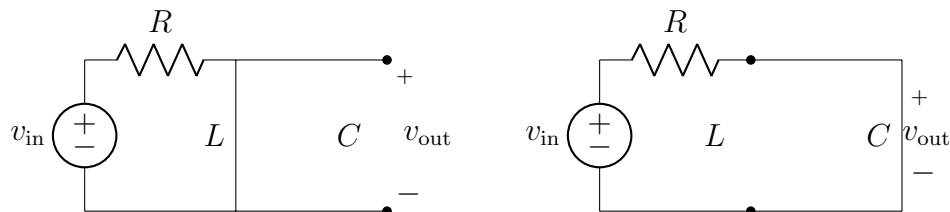- C. Draw equivalent circuits for low frequencies and high frequencies. Use them to verify the extremes of the Bode plot from last week.

Solution:

The left circuit depicts how the original circuit behaves at low frequencies when the capacitor acts like an open circuit and the inductor acts like a short. The right circuit depicts the original circuit at high frequencies when the capacitor acts like a short and the inductor acts like an open circuit. The result in either of these cases is that $v_{out} = 0$.



- D. What is the equivalent impedance of the parallel LC combination at resonance? What can you replace it with?

Solution:


$$Z = Ls \parallel \frac{1}{Cs} = \frac{1}{C} \cdot \frac{s}{s^2 + \frac{1}{LC}}$$

$$Z(j\omega_0) = Z\left(j\frac{1}{\sqrt{LC}}\right) = Ls \parallel \frac{1}{Cs} = \frac{1}{C} \cdot \frac{j\frac{1}{\sqrt{LC}}}{-\frac{1}{LC} + \frac{1}{LC}} = \frac{1}{C} \cdot \frac{j\frac{1}{\sqrt{LC}}}{0}$$

A division by zero indicates that the current will be zero for any voltage across the combination, therefore, the combination acts like an open circuit at resonance.

- E. Draw an equivalent circuit at resonance. Does it correspond to your Bode plot?


Solution:

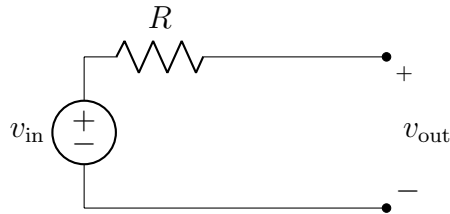

At resonance, $v_{out} = v_{in}$, or $H(s) = 1$ which corresponds to the Bode plot. Note that it would be wrong to draw the L and the C open; neither is open, the parallel combination acts like an open.

Problem 3

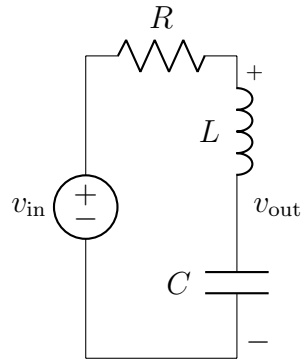- A. Find the transfer function for the circuit shown below using impedances.



Solution:

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{Ls + \frac{1}{Cs}}{R + Ls + \frac{1}{Cs}}$$

$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{1}{L/R}s + \frac{1}{LC}}$$

$$\omega_0^2 = \frac{1}{LC} \quad \alpha = \frac{1}{2L/R}$$

$$H(j\omega) = \frac{\omega_0^2 - \omega^2}{\omega_0^2 - \omega^2 + j2\alpha\omega}$$

B. Sketch the Bode plot of the magnitude of $H(s)$.

Solution:


$$\omega \rightarrow 0 \quad H(j\omega) \approx 1$$

$$\omega \rightarrow \infty \quad H(j\omega) \approx 1$$

At resonance, $\omega = \omega_0$, and the series LC acts like a short.

$$\omega = \omega_0 \quad H(j\omega) = 0$$

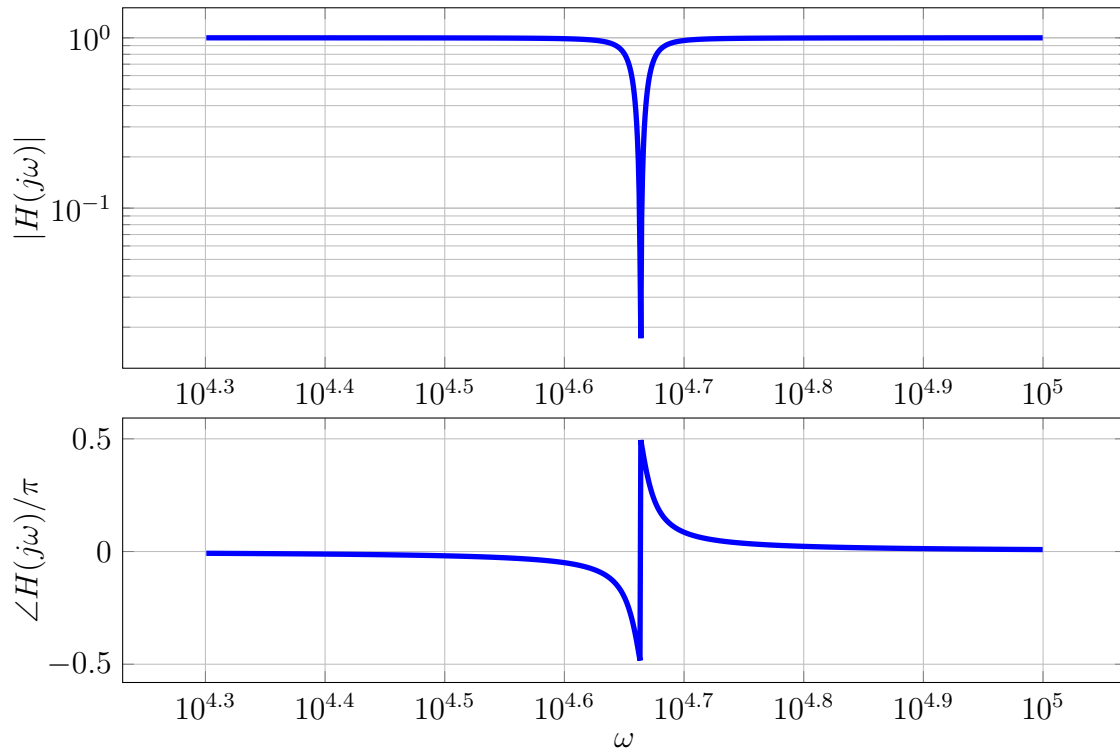
The angle is significantly harder in this case and there is no easy way to get the behavior at resonance. I have included the graph of the angle below. Try to see if you can relate it to the transfer function!



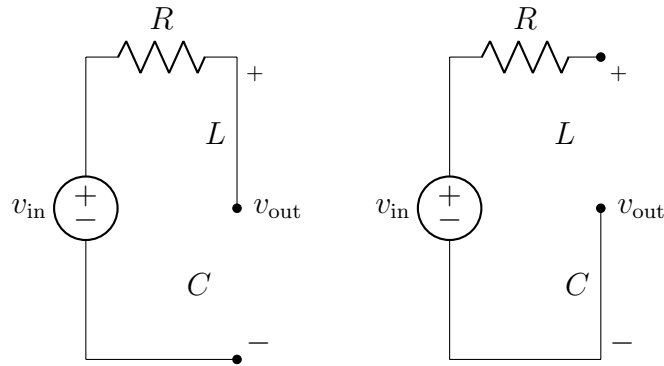- C. Recall that at low frequencies a capacitor may be replaced with an open circuit and an inductor may be replaced with a short circuit and the inverse is true at high frequencies. Draw equivalent circuits for low frequencies and high frequencies. Use them to verify the extremes of the Bode plot.

Solution:


The left circuit depicts how the original circuit behaves at low frequencies when the capacitor acts like an open circuit and the inductor acts like a short. The right circuit depicts the original circuit at high frequencies when the capacitor acts like a short and the inductor acts like an open circuit. The result in either of these cases is that $v_{out} = v_{in}$ as expected, since current flows through R.



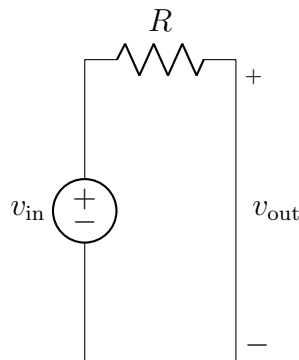- D. Draw an equivalent circuit at resonance.

Solution:

At resonance, $v_{out} = 0$, or $H(s) = 0$.



Course feedback

Feel free to send any additional feedback directly to us.

Name (optional):

- A. End time: How long did the assignment take you?
- B. Are the lectures understandable and engaging?
- C. Was the assignment effective in helping you learn the material?
- D. Are you getting enough support from the teaching team?
- E. Are the connections between lecture and assignment clear?
- F. Are the objectives of the course clear? Do you feel you are making progress towards those objectives?
- G. Anything else?