

**Olin College of Engineering**  
**ENGR2410 – Signals and Systems**

**Assignment 3**

**Problem 1:** (4 points)

- A. Find the equivalent impedance of a series RLC combination.

**Solution:**

$$\begin{aligned} Z &= R + Ls + \frac{1}{Cs} \\ Z &= \frac{s^2 + \frac{1}{L/R}s + \frac{1}{LC}}{s/L} \\ Z &= \frac{1}{Cs} \left( \frac{s^2 + \frac{1}{L/R}s + \frac{1}{LC}}{\frac{1}{LC}} \right) \\ Z &= \frac{L \left( s^2 + \frac{1}{L/R}s + \frac{1}{LC} \right)}{s} \end{aligned}$$

- B. Find an expression for the quality factor  $Q$  of the series RLC in terms of the characteristic impedance  $Z_0 = \sqrt{L/C}$ . Recall that  $Q$  is defined as  $\frac{\omega_0}{2\alpha}$ .

**Solution:**

$$Q = \frac{1}{\sqrt{LC}} L/R = \frac{\sqrt{L/C}}{R}$$

- C. Find a condition for  $R$  such that  $Q \gg 1$ . In the limit, is  $R$  acting more like a short or an open circuit?

**Solution:**

$$R \ll \sqrt{L/C}$$

$R$  is approaching a short.

- D. Repeat the previous three parts for the parallel RLC combination.

**Solution:**

$$Z = R || Ls || \frac{1}{Cs} = R || \frac{Ls}{LCs^2 + 1} = \frac{s/C}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

$$Z = \frac{1}{C} \cdot \frac{s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$


$$Q = \frac{1}{\sqrt{LC}}RC = \frac{R}{\sqrt{L/C}}$$

$$R \gg \sqrt{L/C}$$

R is approaching an open.

**Problem 2:** (6 points)

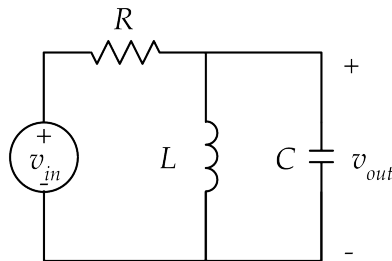A. Find the transfer function for the circuit from last week's problem 2 using impedances.



**Solution:**

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{Ls || \frac{1}{Cs}}{R + Ls || \frac{1}{Cs}}$$

$$H(s) = \frac{\frac{Ls}{LCs^2+1}}{R + \frac{Ls}{LCs^2+1}}$$

$$H(s) = \frac{Ls}{RLCs^2 + Ls + R}$$

$$H(s) = \frac{\frac{1}{RC}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

- B. Show that at low frequencies a capacitor may be replaced with an open circuit and an inductor may be replaced with a short circuit. Show that the inverse is true at high frequencies.

**Solution:**

The complex impedance of a capacitor is  $\frac{1}{Cj\omega}$ . The impedance of the capacitor is related inversely to frequency. At low frequencies  $\omega \rightarrow 0$ , the impedance of the capacitor is really large and the capacitor acts like an open circuit. At high frequencies  $\omega \rightarrow \infty$ , the impedance of the capacitor is really small and the capacitor acts like a short circuit.

$$\lim_{\omega \rightarrow 0} \frac{1}{Cj\omega} = \infty$$

$$\lim_{\omega \rightarrow \infty} \frac{1}{Cj\omega} = 0$$

The complex impedance of an inductor is  $Lj\omega$ . The impedance of the inductor is related directly to frequency. At low frequencies  $\omega \rightarrow 0$ , the impedance of the inductor is really small and the inductor acts like a short circuit. At high frequencies  $\omega \rightarrow \infty$ , the impedance of the inductor is really large and the inductor acts like an open circuit.


$$\lim_{\omega \rightarrow 0} Lj\omega = 0$$

$$\lim_{\omega \rightarrow \infty} Lj\omega = \infty$$

- C. Draw equivalent circuits for low frequencies and high frequencies. Use them to verify the extremes of the Bode plot from last week.

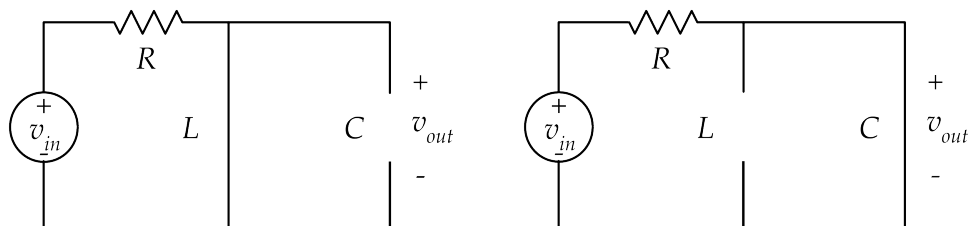**Solution:**

The left circuit depicts how the original circuit behaves at low frequencies when the capacitor acts like an open circuit and the inductor acts like a short. The right circuit depicts the original circuit at high frequencies when the capacitor acts like a short and the inductor acts like an open circuit. The result in either of these cases is that  $v_{out} = 0$ .



- D. What is the equivalent impedance of the parallel LC combination at resonance? What can you replace it with?

**Solution:**


$$Z = Ls \parallel \frac{1}{Cs} = \frac{1}{C} \cdot \frac{s}{s^2 + \frac{1}{LC}}$$

$$Z(j\omega_0) = Z\left(j\frac{1}{\sqrt{LC}}\right) = Ls \parallel \frac{1}{Cs} = \frac{1}{C} \cdot \frac{j\frac{1}{\sqrt{LC}}}{-\frac{1}{LC} + \frac{1}{LC}} = \frac{1}{C} \cdot \frac{j\frac{1}{\sqrt{LC}}}{0}$$

A division by zero indicates that the current will be zero for any voltage across the combination, therefore, the combination acts like an open circuit at resonance.

- E. Draw an equivalent circuit at resonance. Does it correspond to your Bode plot?

**Solution:**

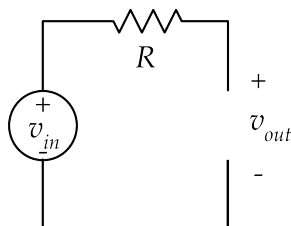

At resonance,  $v_{out} = v_{in}$ , or  $H(s) = 1$  which corresponds to the Bode plot. Note that it would be wrong to draw the L and the C open; neither is open, the parallel combination acts like an open.